

Logic Design (Part 5)

Sequential Logic Devices & Sequential Circuits

Based on slides © McGraw-Hill
Additional material © 2013 Farmer
Additional material © 2014 Narahari

1

Combinational vs. Sequential

•Combinational Circuit

- always gives the same output for a given set of inputs
 - ex: adder always generates sum and carry, regardless of previous inputs

•Sequential Circuit

- stores information
- output depends on stored information (state) plus input
 - so a given input might produce different outputs, depending on the stored information

2

2

Sequential Circuits – The agenda


- Definition of sequential circuits
 - Components of a sequential circuit
- common storage ‘devices’ (built from latches)
 - Register
 - Memory
- synchronization using a **CLOCK**
- Modifying latches to work with a clock...Flip Flops
 - These become the basic unit of storage in sequential circuits
- Designing sequential circuits – methodology
 - Finite state machine diagrams
 - Mapping to truth table.....build circuit

3

3

Sequential Circuit Schematic & State Machine

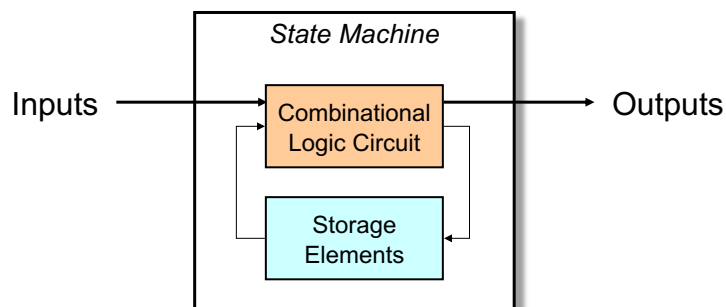- sequential circuit
 - Combines combinational logic with **storage**
 - “Remembers” state, and changes output (and state) based on **inputs** and **current state**



- 1.combinational circuit to compute output and next state
- 2.storage elements to store state

4

4

Sequential Circuits: Finite State Machines

- The behavior of sequential circuits can be expressed using characteristic tables or finite state machines (FSMs).
 - FSMs consist of a set of nodes that hold the states of the machine and a set of arcs that connect the states.
 - Directed graph to represent a FSM
- Moore and Mealy machines are two types of FSMs that are equivalent.
 - They differ only in how they express the outputs of the machine.
 - **Moore machines place outputs on each node/state**
 - Associate an output with each state
 - Mealy machines present their *outputs on the transitions*.

5

5

FSM Design Process

- The first step is to model the behavior of the machine
 - Based on problem statement
 - Identify what the inputs are
 - Identify the outputs
 - Determine what needs to be stored to capture the “state” of the machine
- Represented as a graph – finite state diagram
 - Nodes: States – a state stores summary of events (until current time)
 - Edges: Transition from current state to next state
 - Based on input and current state
 - Computed by combinational logic
 - Outputs: Using Moore machine, determine value of outputs at each state

6


6

Design a Counter: counts from 0 to 7

7

7

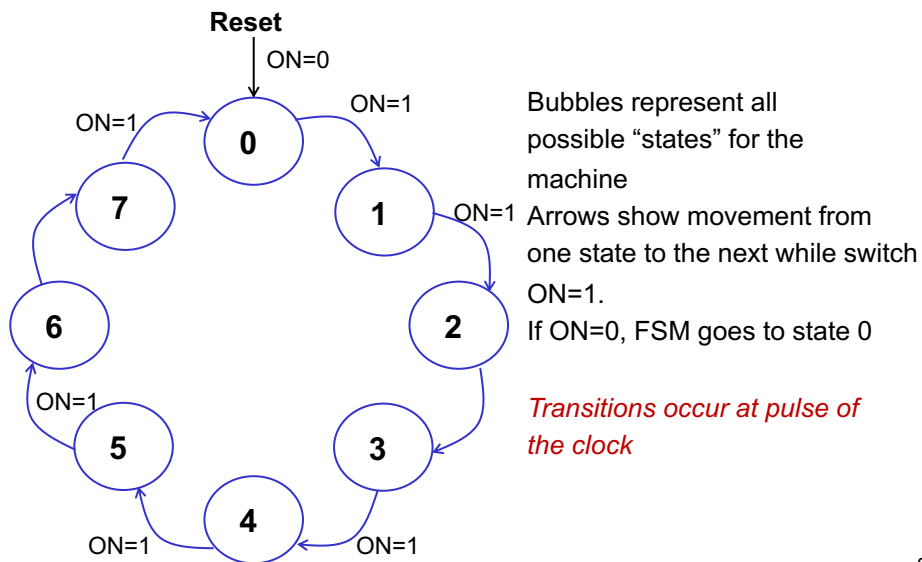Finite State Machine Representation of Counter: Counter to count from 0 to 7 (while switch is ON)



8

8

Example: A Vending Machine

- Accept user input (coins), when total is at least 50 cents dispense output (candy)
 - We will not model the change to be returned, and only care if the input is at least 50 cents
- Input valid coins:
 - Q (25cents) D (10) or N (5)
- What should it keep track of ?
 - current total
 - Is it 50 cents or more ?
- When it reaches 50 or more:
 - Generate output
- States of the machine ?
 - What should each state capture ?
 - How many states ?

9

9

Sequential Logic

- Where do we start:
- Build a device, using combinational logic devices, to **store** a value...*done!!*
 - D Latch (and RS Latch) – stores 1 bit
 - concept of memory
- Build other storage devices using the D Latch and logic devices we have at our disposal (i.e., in our *library*)
- What is the methodology behind design of sequential logic circuits
 - Finite State Machines to Truth Tables to Circuit
- Combine sequential and combinational logic devices to “assemble” a simple processor!

10

10

Latches and Flip-Flops and Clock

- Latch: basic circuit for storage
 - Operate on changes in Level (i.e., 1 or 0)
 - D-Latch can store 1 bit
- Flip-flop:
 - Sequential circuits take input from output of storage
 - Latches that work on change of level can lead to unstable sequential circuits
 - As level changes the outputs change --- inputs change!
 - Flip-Flop circuits designed to operate properly when they are part of a sequential circuit
 - Modify D Latch to get a D Flip Flop (DFF)
 - Flip Flop changes state at the 'instant' that the level changes
- Clock:
 - Need to coordinate and synchronize when states change...
 - Use Clock to enable or disable the devices in a timed manner

11

11

Our Latches


- We have designed two devices capable of storage
- RS Latch
 - Cross coupled NAND gates
 - Two inputs S (set) and R (reset) and Two outputs Q and Q'
- D Latch
 - Built from RS Latch
 - Two inputs D (value to be set), WE (write enable) and two outputs Q and Q'

12

12

Recall the Gated D-Latch: Our 1-bit storage element

 
- Add logic to an R-S latch
 - Create a more convenient interface, prevent $S=0 \ \&\& \ R=0$
- Two inputs: D (data) and WE (write enable)
 - When $WE = 1$, latch is set to value of D
 - $S = \text{NOT}(D), R = D$
 - When $WE = 0$, latch continues to hold previous value
 - $S = R = 1$ (hold condition for SR latch)
- Extra logic does not allow $S=0, R=0$ case to occur



13

Next... Storage Devices

 - we now have a device (D-Latch) that can store a bit
 - Abstract the device: input D, WE; output/storage Q




- Use this to build 'real' storage devices....
- Temporary storage in a computer...Register
 - Where are variables stored before being sent to the arithmetic unit for operations on them?
 - Can we build an n-bit register using latches?
- What about "main" memory
 - Memory hierarchy ?

14

14

Multi-Bit D-Latch: Register ?

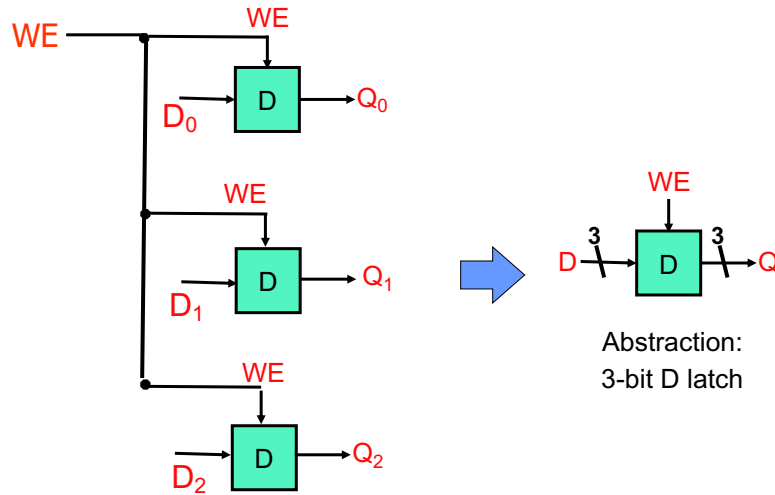
- A collection of D-latches, controlled by a common WE
- When WE=1, 3-bit value D is written to the outputs



15


Multi-Bit D-Latch – Register: Inside the latches

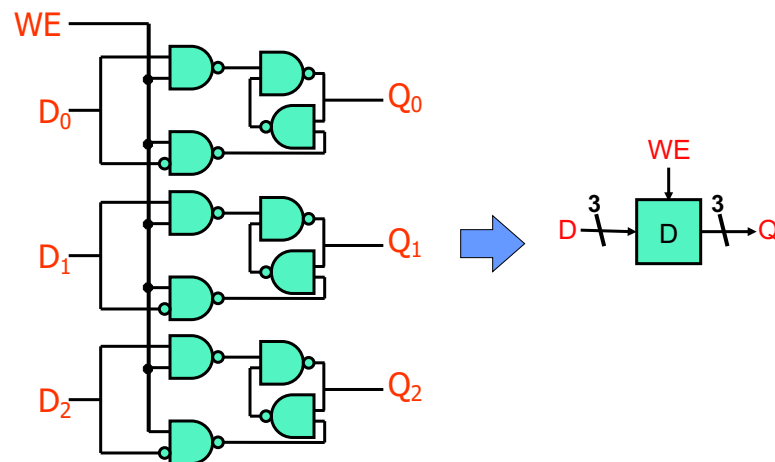- A collection of D-latches, controlled by a common WE
- When WE=1, n-bit value D is written to the outputs



16

Recall: A Basic Model of a Computer

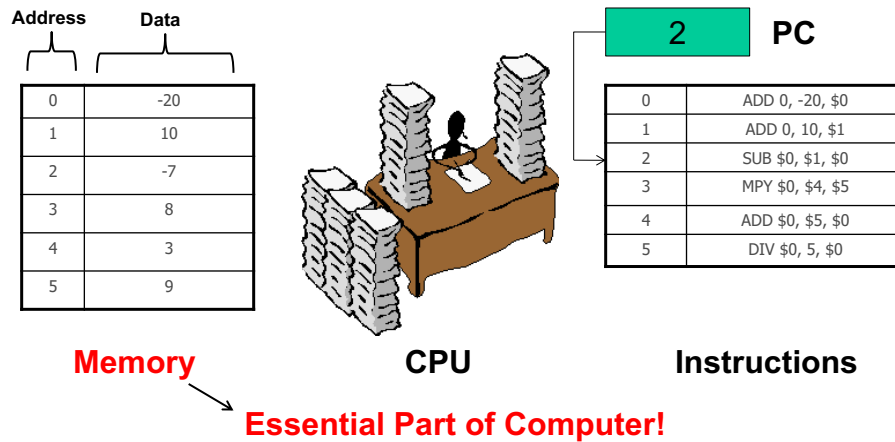

Basic Components: Address: Looks up data
Note: both are in binary

17

17

Memory

- We know how to store m-bit number in a register
- How about many m-bit numbers?
 - Bank of registers?
- How to fetch a specific m-bit number?
 - **addressing**

18


18

Memory

- Now that we know how to store bits, we can build a memory – a logical k by m array of stored bits

Address Space:
number of locations
(usually a power of 2)

$k = 2^n$
locations

 

Addressability:
number of bits per location
(e.g., byte-addressable)


m bits

19

19

Memory Interface

- ❖ There are two basic operations on a memory
 - Selecting one of the memory locations to **read** from
 - Selecting one of the memory locations to **write** to
- ❖ Interface signals
 - A: n -bit address lines to select/specify a location
 - D_{out} : Contents of selected location during read (m bits)
 - D_{in} : Value to be stored during write (m bits)
 - WE: If WE = 1 then write operation, WE = 0, read operation

 


20

20

Memory

 - Looking from the outside, what do we need?



21

21

Memory

A large number of addressable fixed size locations

- Address Space

n bits allow the addressing of 2^n memory locations.

- Example: 24 bits can address $2^{24} = 16,777,216$ locations (i.e. 16M locations).
- If each location holds 1 byte (= 8 bits) then the memory is 16MB.
- If each location holds one word (32 bits = 4 bytes) then it is 64 MB.

22

22

Memory


- Addressability
 - Computers are either **byte** or **word** addressable - i.e. each memory location holds either 8 bits (1 byte), or a full standard word for that computer (16 bits for the LC-3, more typically 32 bits, though now many machines use 64 bit words).
- Normally, a whole word is written and read at a time:
 - If the computer is **word** addressable, this is simply a single address location.
 - If the computer is **byte** addressable, and uses a multi-byte word, then the word address is conventionally either that of its most significant byte (**big endian** machines) or of its least significant byte (**little endian** machines).

23

23

Memory

 - READ operation: Given address A of N bits, fetch contents at that address
 - From 2^N locations we *select* one of them to be sent to the output
- WRITE: Given address A of N bits, write into exactly one of the 2^N locations.



24

24

Devices to construct Memory ?

- To store a m-bit number use a "register" (m-bit D-latch)
 - To store 2^N of these m-bit numbers, use 2^N m-bit latches
- For READ: what is the device that can send one out of 2^N inputs (inputs are in the 2^N latches) ?
- For WRITE: what is the device that can enable exactly one Write Enable (WE) from the 2^N D-latches ?

25

25


2^2 by 3-bit memory

- Read operation

But how do we select/enable ONE of the D-latches to send to the output?
Given 2 bit address,
Select ONE latch

2^2 or 4 registers

Selects "address" to read

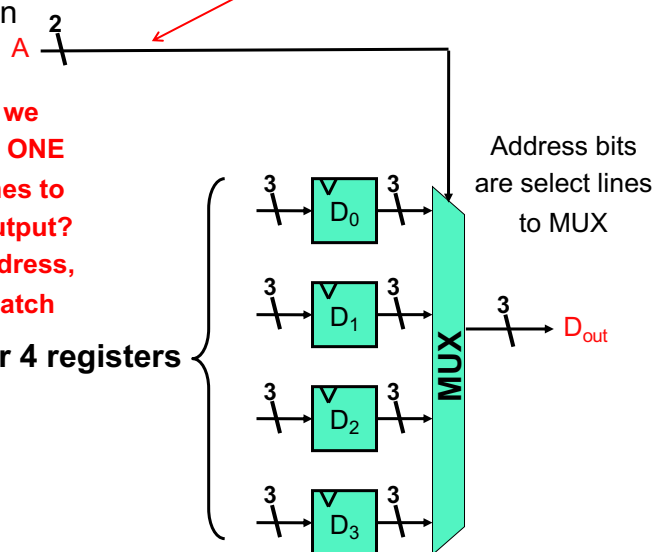

26

26


2² by 3-bit memory

- Write operation

How do we enable write into exactly one memory location

Use 2-4 Decoder:
Input address bits= A,
exactly one D-latch
has WE=1

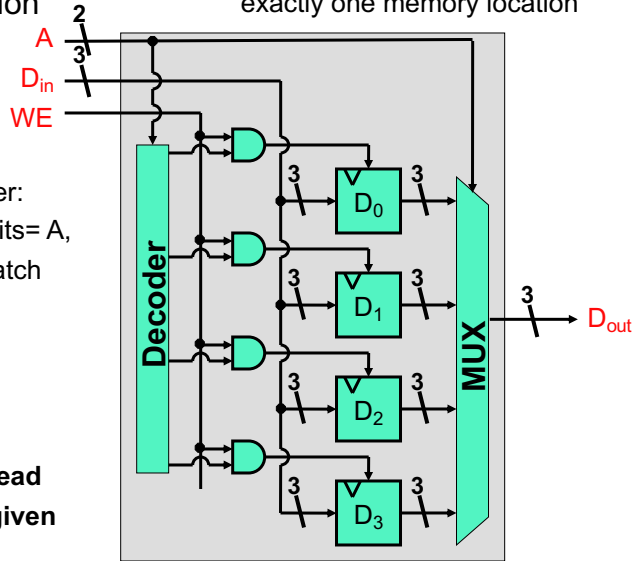Limitation:
You can only read
or write at any given
time



27


27

2² by 3-bit memory - Multiple “Ports”

- Independent Read/Write

You can read from one
address and write to
another with this
arrangement

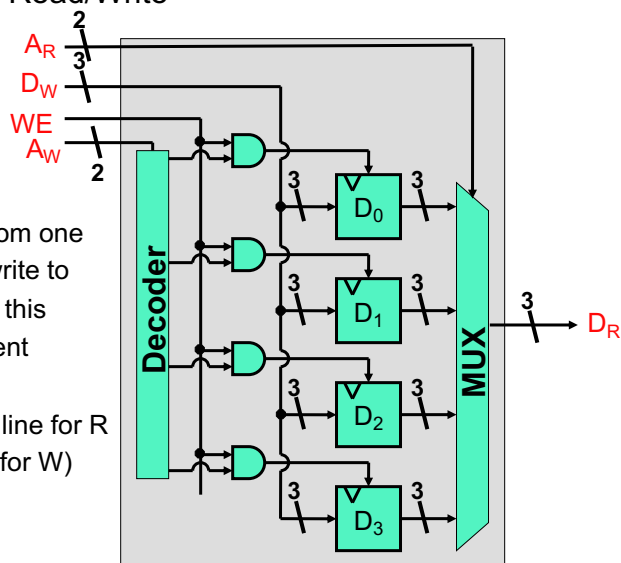
(notice 1 address line for R
1 address line for W)



28


28

2² by 3-bit memory - Multiple Read Ports

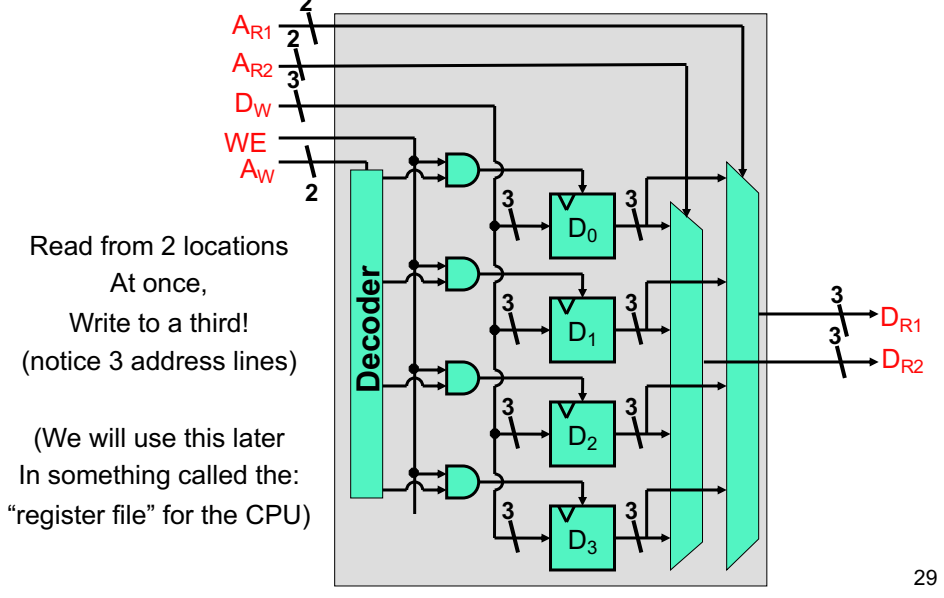

29

 Inside an Efficient 2² by 3-bit Memory - Single Port



30

More Memory Details

- This is still not the way actual memory is implemented
 - Real memory: fewer transistors, denser, relies on analog properties
- But the logical structure is similar
 - Address decoder
 - Word select line, word write enable
 - Bit line
- Two basic kinds of **RAM** (Random Access Memory)
 - **Static RAM** (SRAM) - 6 transistors per bit
 - Fast, maintains data as long as power applied
 - **Dynamic RAM** (DRAM) - 1 transistor per bit
 - Denser but slower, relies on “capacitance” to store data, needs constant “refreshing” of data to hold charge on capacitor

Also, non-volatile memories: ROM, PROM, flash, ...


31

31

Dynamic RAM

- Information stored as charge on capacitors.
- Capacitors leak so values have to be ‘refreshed’ continually
- As memory chips get larger, access times tend to increase. The processor spends more time waiting for data.

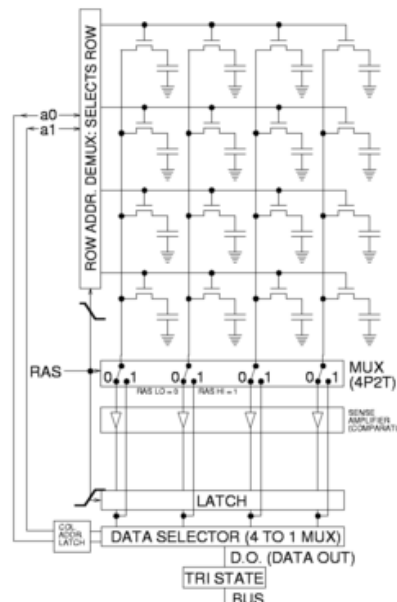➤ This is a **major** issue limiting computer systems performance



32

Speed mismatch: Example

- Intel Core i5 – Processor
 - Clock rates approx 2.5GHz, Clock period approx 0.4 ns
- DDR2-667 PC2-5300 SO-DIMM – 2 GB Memory
 - Can deliver at most 1 64-bit word every 1.5 ns
- Mismatch between processor speed and memory speed




33

33

Memory Hierarchy

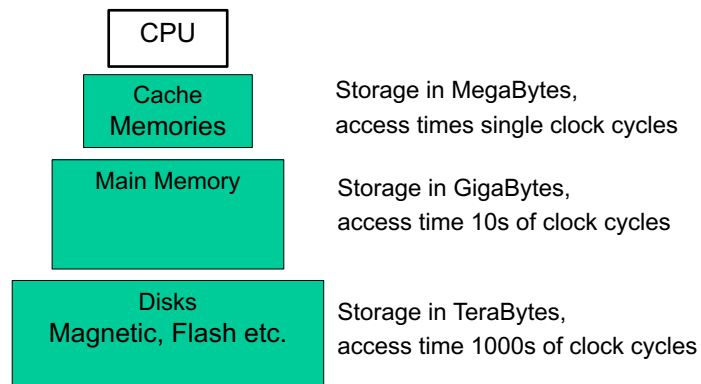- Modern computers try to mitigate memory delays by exploiting locality of reference through caches.
- Smaller, faster memory stores are placed closer to the CPU and bulk transfers from slower memory are used



34

34

Memory Hierarchy

- Will return to this at the end of the course....!

35

35

Are we ready to design sequential circuits and finite state machines ?

- Is something missing ?
- When do states change in a machine ?
- Do we let states change at arbitrary times ?
- What do you think happens in a computer ?

36

36


Clocked Flip-Flops/Circuits

- Subsystem in a computer consists of a large number of combinational and sequential devices
 - Each sequential device is like latch which is in one of two states
 - As machine executes its cycle, the states of all sequential devices change with time
- To control large collection of devices in an orderly (synchronized) fashion, machine maintains a **clock**
 - Requires all devices to change their states at the same time
 - Clock generates sequence of pulses
- Much easier to design, debug, implement, and test
- How do we change latches so that they allow change in state synchronized with the clock ?
- Sequential logic circuits require a means by which events can be sequenced.....clock!

37

37


Introducing - The Clock!

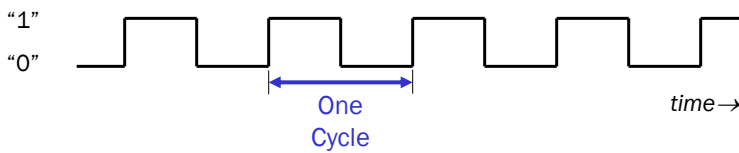- A **clock** controls when stored values are “updated”
 - Electrical waveform – sends pulses through a circuit
 - Changes values at a periodic rate
- 
- The clock will act as the ‘heartbeat’ of our system
 - The number of cycles per second is the **clock frequency** measured in cycles per second or Hertz (Hz)
 - The **clock period** refers to the duration of one clock cycle. The period and frequency are inversely related.
 - Typical clock frequency: $2.5\text{GHz} = 2.5 \times 10^9 \text{ Hz}$
 - So corresponding clock period = $1/(2.5 \times 10^9) = .4 \times 10^{-9} \text{ sec}$
 - That would be: 0.4 nanoseconds

38

38


Attaching Clock to D-Latch

 

- Attach CLOCK to the WE on D-Latch
- We create “windows” of time that we can store data into latch
 - When the CLOCK is “HIGH” – D-latch is open
 - When the CLOCK is “LOW” – D-latch is closed
- D=Q while CLOCK is High
- We have to prepare what we wish to store, right before latch closes

Oops...changes in input while clock=High cascade to output Q

 
- Q can change multiple times during clock cycle: not synchronized with clock



39

Why Clocked D-latches may not work

- Sequential circuit: the next state (and output) depend on values of current state and input
- If input to D-latch changes while clock is High, then next state (and output) can change during this single clock cycle
 - state we want to store as next state could be overwritten
- we want to force changes (in state and input) to be synchronized to the clock
 - allow input/states to be read and output/next state to change ONCE per clock cycle

 

40

40

Enter the Flip Flop....

- Flip flops are edge triggered devices
 - They capture the input and change state when the clock changes level
 - Positive edge triggered: when clock goes from 0 to 1
 - Negative edge triggered: when clock goes from 1 to 0
- We refer to the D flip flop as an **edge-triggered** device.
 - D=Q ONLY when WE changes from 0 to 1
- This differs from D latch, which is: **level-triggered**
 - D=Q anytime WE equals 1


41

41


D Flip-Flop vs. D-Latch – Timing Diagrams

Observe difference in how output Q synchronizes with clock edge in DFF

Timing Diagram for D-Latch:

 

Timing Diagram for DFF:

 


42

42

D Flip-Flop

• D Flip-Flop is a pair of D latches

 - Isolates *next* state from *current* state
- Output of DFF read when clock is high, Next state stored end of cycle




• Two phases:

- Clock = 1: $WE_1 = 0$: Latch #1 closed, $WE_2 = 1$: Latch #2 open
- Clock = 0: $WE_1 = 1$: Latch #1 open, $WE_2 = 0$: Latch #2 closed

43

43

D Flip-Flop timing Diagram

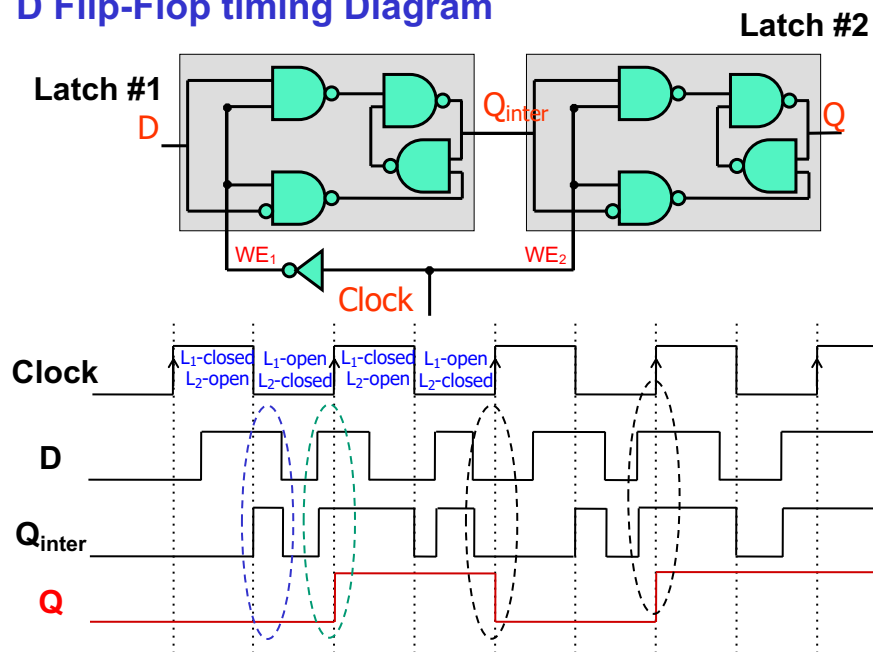

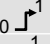

44


44

D Flip-Flop

- We can think of the D Flip-Flop as a 1 bit storage container with an input, D, and an output, Q and connected to a clock input
- A set of D flip-flops can be grouped together with common Clock and WE inputs to form a **register** -- replace D-latch with D flip flop

Truth table for DFF:
X = don't care (i.e, 0 or 1)


| D | Clk | Q |
|---|---|--------|
| 0 | 0  | 0 |
| 1 | 0  | 1 |
| X | 0 | Last Q |
| X | 1 | Last Q |

 


45

45


Our basic "Storage" Devices

 

 RS Latch – Stores 1 Bit, Level-Triggered
-1 "forbidden" input: S=0, R=0
-Holds Data when RS=11



 D-Latch – Stores 1 Bit, Level-Triggered
-No "forbidden" inputs (fixes RS Latch)
-D=Q when WE=1
-Holds Data when WE=0



D-Flip-Flop – Stores 1 Bit, Edge-Triggered
-No "forbidden" inputs
-D=Q when WE (CLK) transitions from 0 to 1
-Holds Data for WE=1 or WE=0
-Except when WE transitions from 0 to 1


46

46

One more tweak...

D Flip-Flop with Additional Write Enable

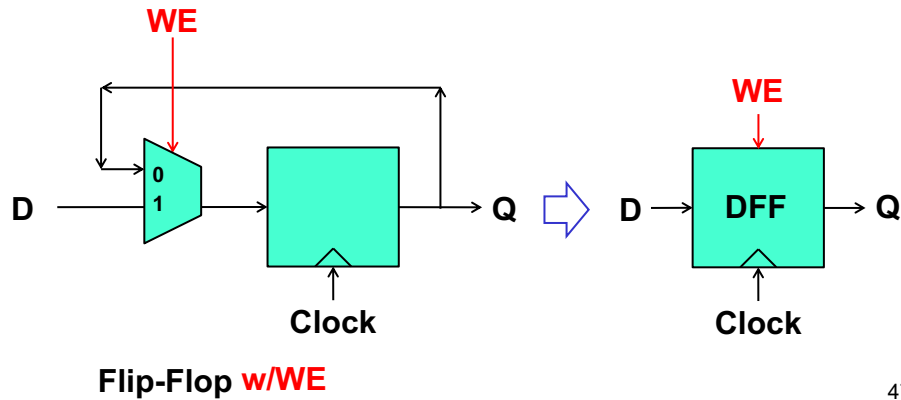
- From previous slides, we attached clock to WE of the D-flip-flop
- Now, we add another WE line to the flip flop
 - Just holds onto data already stored in DFF
- Give it the ability to “ignore” the clock!



47

47

Schematic of a Sequential Circuit

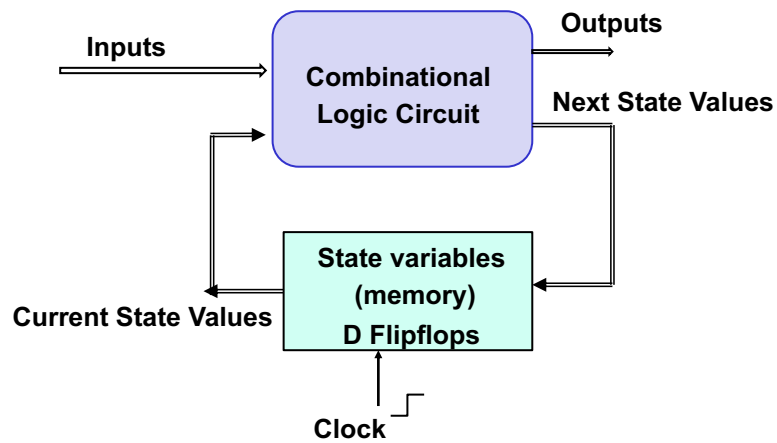

48

48

Next: Design methodology for sequential logic circuits .. Finite State Machines

- We have storage devices and method for synchronization
 - Flip flops and Clock
- How do we design a clocked circuit to solve our problems ?
 - Example: Is there a methodology behind designing a circuit to implement a Counter ?
- Provide procedure for designing Sequential circuits (to implement Finite State Machine)
 - Storage Device to store state: D flip flop
 - Logic to implement next state: combinational gates/devices
 - How to derive the logic: truth tables

49

49

States in a FSM

- The concept of state
 - the **state** of a system is a “**snapshot**” of all relevant elements at a moment in time.
 - a given system will often have only a **finite number of possible states**.
 - For many systems, we can define the rule which determines under what conditions a system can **move from one state to another**.
 - So when do they change states ?
 - Synchronized to clock (edge triggered)
- Determining the ‘states’
 - Problem statement determines what information needs to be stored (state is a summary)
 - How many states does the machine need ?

50

50


Designing and implementing a FSM

1. First draw the state diagram
 - Encode each state in binary using N bits
 - These N bits correspond to N “state variables” that need to be stored. Call them $S_{N-1} S_{N-2} \dots S_1 S_0$
 - State diagram will show transitions from state to state based on value of inputs
2. Next, derive the truth table (from state diagram)
 - “inputs” in truth table are N current state variables and the inputs
 - “outputs” are the values of the state variables in the next state and the output at each state -- common notation is S' but confusion with complement operator, so let's use S^*
3. From truth table, derive combinational circuit (boolean function) for each of the next state values
 - State variables are stored in your N storage elements

51

51

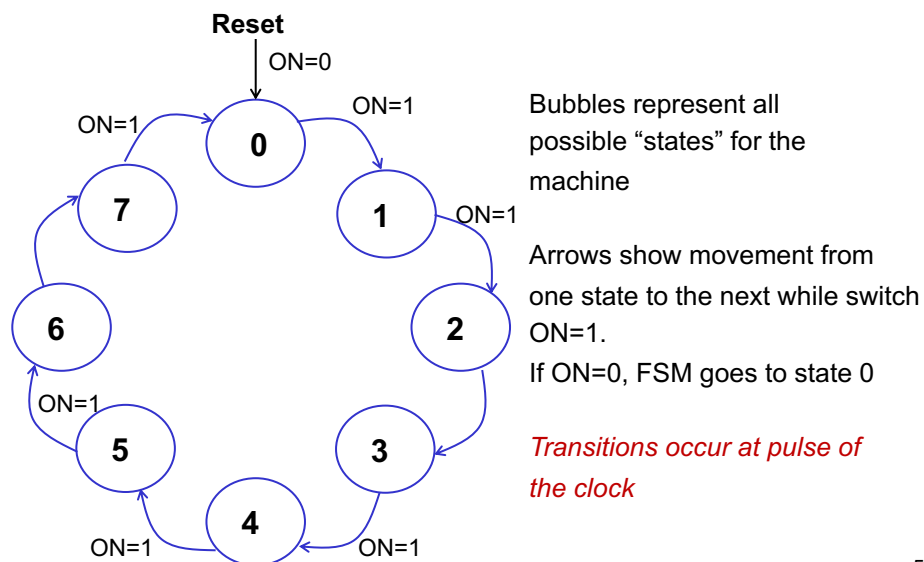
Finite State Machine Representation of Counter: Counter to count from 0 to 7 (while switch is ON)



52

52

Labelling States in Binary

 

We have 8 states, therefore we need $\log_2 8 = 3$ bits to encode states in binary:
from 000 to 111

Each bit is called a state variable & Stored in one D flip flop
we need 3 Flip flops to store 3 bits $S_2 S_1 S_0$

53

53

Storage

- Each D flip flop stores one state bit.
- The number of storage elements (flip-flops) needed is determined by the number of states (and the representation of each state).
 - Each bit can be 0 or 1 = 2 states
 - N bits can represent 2^N states
- Example: If FSM has 12 states, then circuit needs $\log_2 12 = 4$ storage elements (i.e., flip flops).
 - Fewer the states, less hardware needed
 - *Concept of Minimization of States for a given FSM...*
 - ...in Foundations (where else!!)

54

54

Designing and implementing a FSM

1. First draw the state diagram
 - Encode each state in binary using N bits
 - These N bits correspond to N “state variables” that need to be stored. Call them $S_{N-1} S_{N-2} \dots S_1 S_0$
 - State diagram will show transitions from state to state based on value of inputs
2. Next, derive the truth table (from state diagram)
 - “inputs” in truth table are N current state variables and the inputs
 - “outputs” are the values of the state variables in the next state S^* and the output at each state (common notation is S' but confusion with complement operator, so let's use S^*)
3. From truth table, derive combinational circuit (boolean function) for each of the next state values
 - State variables are stored in your N storage elements

55

55

Truth Table Representation of Counter

| Input | Present State | | | Next State | | |
|-------|---------------|----------|----------|--------------|--------------|--------------|
| | $S_2(t)$ | $S_1(t)$ | $S_0(t)$ | $S_2^*(t+1)$ | $S_1^*(t+1)$ | $S_0^*(t+1)$ |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 0 |
| 1 | 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 |
| 0 | X | X | X | 0 | 0 | 0 |

56

56

Designing and implementing a FSM

1. First draw the state diagram
 - Encode each state in binary using N bits
 - These N bits correspond to N “state variables” that need to be stored. Call them $S_{N-1} S_{N-2} \dots S_1 S_0$
 - State diagram will show transitions from state to state based on value of inputs
2. Next, derive the truth table (from state diagram)
 - “inputs” in truth table are N current state variables and the inputs
 - “outputs” are the values of the state variables in the next state and the output at each state -- common notation is S' but confusion with complement operator, so let's use S^*
3. From truth table, derive combinational circuit (boolean function) for each of the next state values
 - State variables are stored in your N storage elements

This part is no different from combinational circuit design!

57

57

Boolean functions for values of next state

- For each state variable, derive function that determines next state for that variable:
- Note: $S_2(t+1)$ – value of state variable at time (t+1) is denoted as S_2^*
- Current states: $S_2 S_1 S_0$
- Derivation here is only for case when $On=1$


- $S_2^* = On.(S_2' S_1 S_0 + S_2 S_1' S_0' + S_2 S_1' S_0 + S_2 S_1 S_0')$

- $S_1^* = On.(S_2' S_1' S_0 + S_2' S_1 S_0' + S_2 S_1' S_0 + S_2 S_1 S_0')$

- $S_0^* = On.(S_2' S_1' S_0' + S_2' S_1 S_0' + S_2 S_1' S_0' + S_2 S_1 S_0')$

58

58

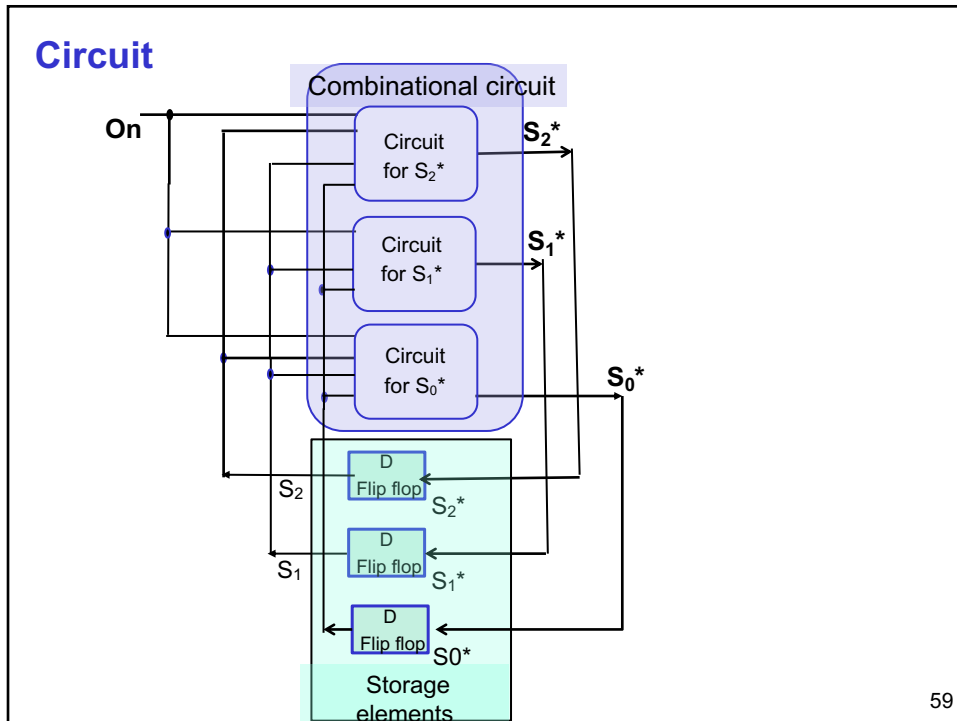

59

Summary: Designing and implementing a FSM


1. First draw the state diagram
 - Encode each state in binary using N bits
 - These N bits correspond to N “state variables” that need to be stored. Call them $S_{N-1} S_{N-2} \dots S_1 S_0$
 - State diagram will show transitions from state to state based on value of inputs
2. Next, derive the truth table (from state diagram)
 - “inputs” in truth table are N current state variables and the inputs
 - “outputs” are the values of the state variables in the next state and the output at each state -- common notation is S' but confusion with complement operator, so let's use S^*
3. From truth table, derive combinational circuit (boolean function) for each of the next state values
 - State variables are stored in your N storage elements

60

60

 Example 2: Blinking Traffic Sign: Start all lights off – lights bulbs 1,2,3,4,5 off


- (from textbook) Design control circuitry for a blinking traffic sign (to show “move right” message)



61

61


Step2: switch ‘on’ 2 lights – bulbs 1,2

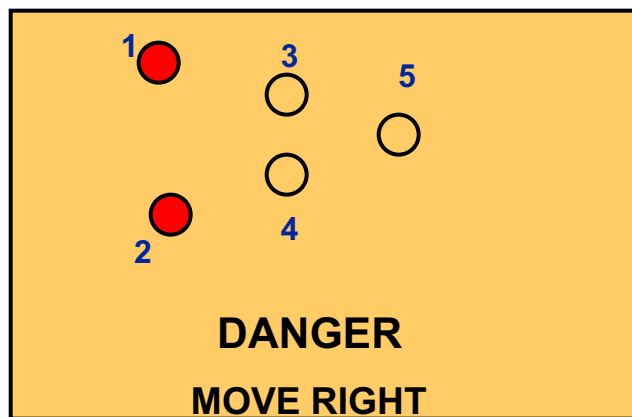

62

62

 
Step 3: Switch 'on' 4 lights – bulbs 1,2,3,4



63

63


Step 4: switch 'on' 5 lights – 1,2,3,4,5

 

64

64

 **Step 5- switch all 'off' – lights bulbs 1,2,3,4,5 off
And repeat the cycle**



65

65


Example: Traffic Sign

- A blinking traffic sign: How many lights/lightbulbs = 5
- How many states ?
- 4 states
 - No lights on
 - 1 & 2 on
 - 1, 2, 3, & 4 on
 - 1, 2, 3, 4, & 5 on
 - (repeat as long as switch is turned on)
- How many bits to represent the 4 states
- S_1S_0
 - With S_1S_0 values: 00, 01, 10, 11
- How many 'outputs' (to control the 5 lights) = 5 ?
- If the sign is switched off then all lights turn off

66

66

Traffic Sign State Diagram

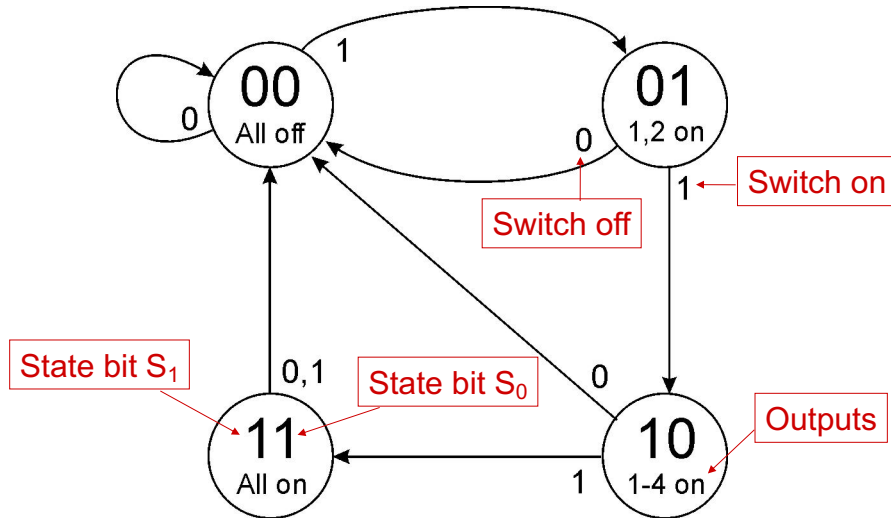

Transition on each clock cycle.

67


67

Outputs

- Note we really have 3 groups of lights to be controlled = 3 control lines X,Y,Z
 - Group 1: Lights 1 and 2; controlled by Z
 - If Z=1 then Group 1 lights (1 and 2) are switched on
 - Group 2: lights 3 & 4; controlled by Y
 - Group 3: Light 5; controlled by X
- In this example, we associate each state with an output
 - Depending on the current state, we switch on specific groups of lights

68

68

 

69

- When is group 1 on?
 - in states 01, 10 and 11 - but only when the switch IN is on!
- Logic expressions for X,Y,Z
 - Depends on S_0 and S_1 and Input is on
 - If Input is off then X,Y,Z are all 0
- can you come up with a logic expression for next state values of S_0 and S_1 ?
 - Depends on current values of S_0 and S_1 and Input is on
 - Input off then both bits are set to 0 since next state is 00
 - Next state value of S_0 denoted $S'_0 = 1$ if current state is 00 or current state 10 and $In=1$
- When do we switch to the next state?
 - the two bits of $S[1:0]$ are updated at every clock cycle
 - we have to make sure that the new state does not propagate to the combinational circuit input until the next clock cycle.

70

70

Traffic Sign Truth Tables

Outputs
(depend only on state: S_1S_0)

| S_1 | S_0 | Z | Y | X |
|-------|-------|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

Lights 1 and 2
Lights 3 and 4
Light 5

Next State: $S_1'S_0'$
(depend on state and input)

| In | S_1 | S_0 | S_1' | S_0' |
|----|-------|-------|--------|--------|
| 0 | X | X | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 |

Switch

Whenever In=0, next state is 00.

71

71

Boolean functions for light control bits

- from truth table, consider all rows where outputs =1

- $Z = ((\text{NOT } S_1)S_0 + S_1(\text{NOT } S_0) + S_1S_0).In$


- $Y = (S_1S_0 + S_1(\text{NOT } S_0)).In$

- $X = (S_1S_0).In$

72

72

Traffic Sign Logic

 

73

73

Exercise: Design a sequential circuit

- Counter that counts from 0 to 6
 - Resets to 0 after 6
 - Keeps going as long as "input" = 1
 - Ignore this for now
- Finite state diagram
- Truth table
- Logic functions for next state

74

74

Summary of Digital Logic

- Combinational logic
 - Basic gates
 - Combinational devices
- Sequential logic
 - Storage element... Flip flop
 - Theory behind design of finite state machines
 - They act like controllers of a circuit
- Sequential logic devices
 - Memory, ROM, RAM, Registers

So, what is the purpose of all this ?.....

75

75

The Agenda

- Take the elements that we have encountered so far
 - Combinational Elements
 - Gates, Adders, Muxes, decoders
 - Storage Elements
 - Flip flops, registers, memories
- And use them to build a circuit that can perform a **sequence** of arithmetic operations.
 - In essence, we will build a very simple CPU

76

76

From Logic to Processor Design

•Combinational Logic

- Decoders -- convert instructions into control signals
- Multiplexers -- select inputs and outputs
- ALU (Arithmetic and Logic Unit) -- operations on data

•Sequential Logic

- State machine -- coordinate control signals and data movement
- Registers and latches -- storage elements

77

77

Next: Putting it all together

- The goal:
 - Turn a theoretical device - Turing's Universal Computational Machine - into an actual computer ...
 - ... interacting with data and instructions from the outside world, and producing output data.
- Smart building blocks:
 - We have at our disposal a powerful collection of combinational and sequential logic devices.
- Now we need a master plan ...
 - We need to start with defining the model of a computer architecture
 - **Von Neuman model**

78

78